

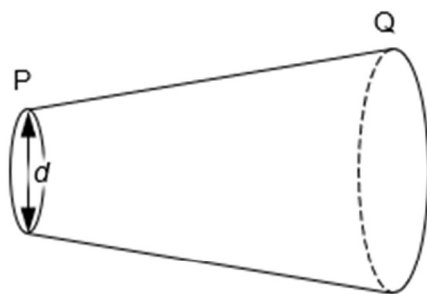
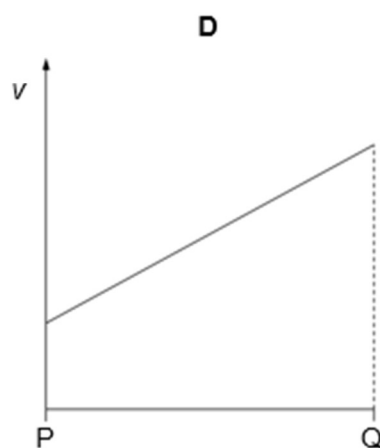
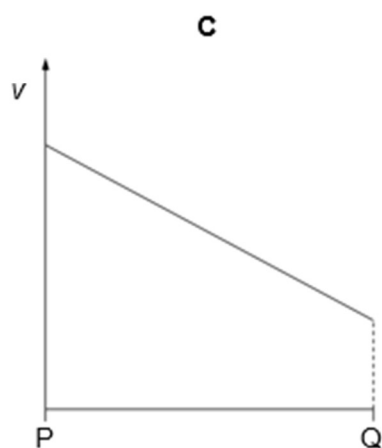


1

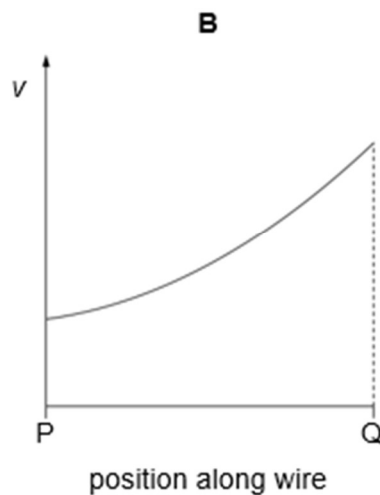The diameter d of a wire PQ increases linearly with distance along the wire from end P to end Q. There is current I in the wire.



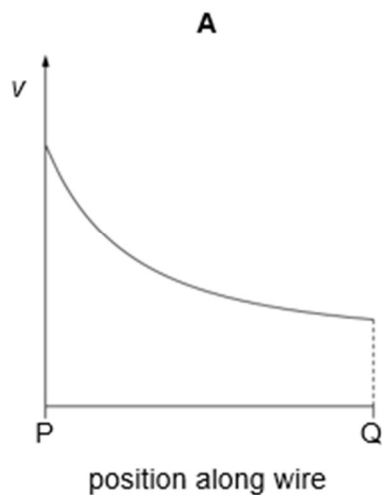Which graph shows the variation of the average drift speed v with position along the wire between P and Q?




2

The current I through an electrical component is measured when a potential difference V is applied across it.

The graph shows the variation of I with V .

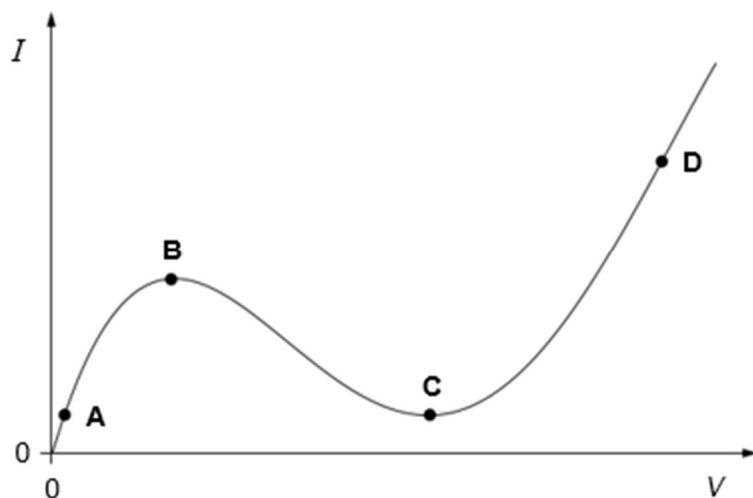At which point is the resistance the greatest?



3

Protons in a parallel beam each move at a uniform velocity v , thus forming a current I . the charge on each proton is e .

Which expression represents the number of protons present in unit length of the beam?


A $\frac{I}{e}$

B $\frac{I}{ev}$

C $\frac{Iv}{e}$

D $\frac{I}{v}$

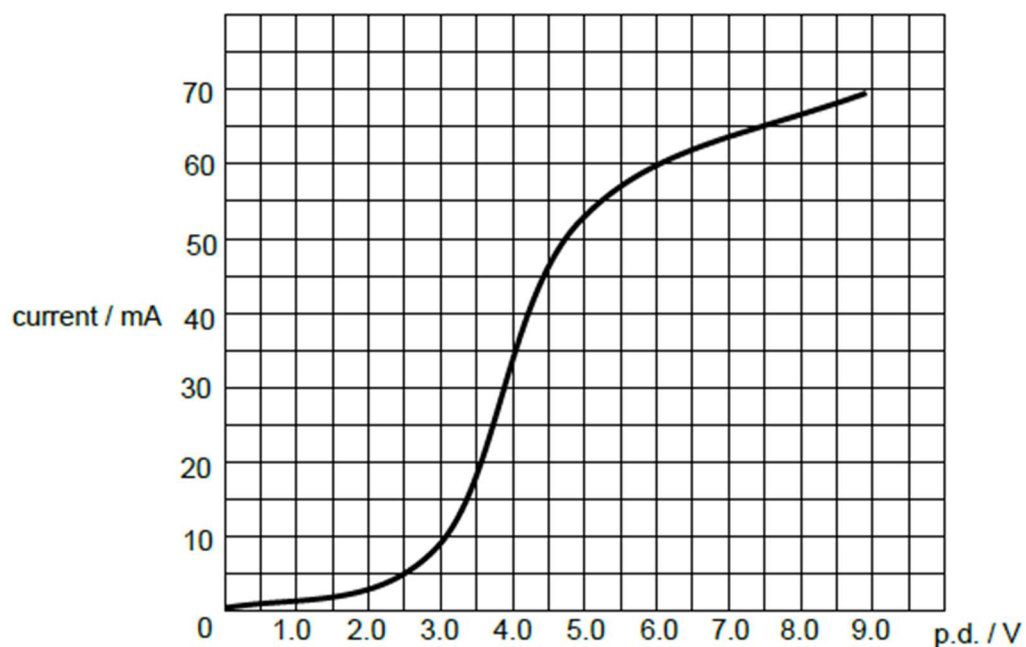
- 7 A graph of current against potential difference for a component is given below.



What is the potential difference across the component when its resistance is at its lowest?

- A** 1.5 V **B** 4.0 V **C** 5.0 V **D** 7.0 V

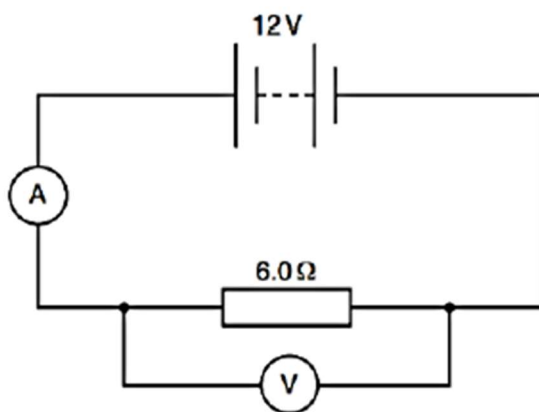- 8 In the circuit shown, the battery is ideal but the ammeter and voltmeter are **not** ideal.



The ammeter reads 1.9 A while the voltmeter reads 11 V.

What are the resistances of the ammeter and voltmeter?

	resistance of ammeter / Ω	resistance of voltmeter / Ω
A	0.32	170
B	0.32	8.3
C	0.53	170
D	0.53	8.3

- 9 An ideal cell is connected across a resistor for an unknown period of time.

Which quantities can be used to calculate the energy supplied by the cell?

- A The current in the resistor and the resistance of the resistor.
- B The current in the resistor and the potential difference across the resistor.
- C The total charge passing through the resistor and the resistance of the resistor.
- D The total charge passing through the resistor and the potential difference across the resistor.


- 10 A battery is connected in series with a resistor R . The battery drives 1500 C of charge completely round the circuit. During this process, 2500 J of energy is dissipated in the resistor R and 500 J is dissipated in the battery.

What is the e.m.f. of the battery?

- A 0.50 V B 0.33 V C 1.7 V D 2.0 V

11

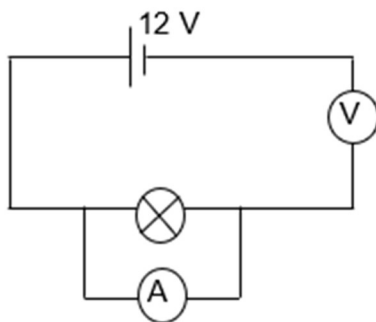An ammeter and a voltmeter are connected to a bulb of resistance $4.0\ \Omega$ as shown below.



Which of the following situations is most likely to happen?


- A Ammeter will fuse.
- B Ammeter reads 3.0 A and voltmeter reads 12 V .
- C Ammeter reads zero current and voltmeter reads 12 V .
- D Both ammeter and voltmeter give zero readings.

12

A new rechargeable battery has the marking " 500 mA h " printed on it. Which of the following is correct with regards to the battery?

- A The e.m.f. of the battery is 500 V .
- B The current from the battery is always 0.5 A .
- C The energy stored in the battery is 1800 J .
- D The charge stored in the battery is 1800 C .

13

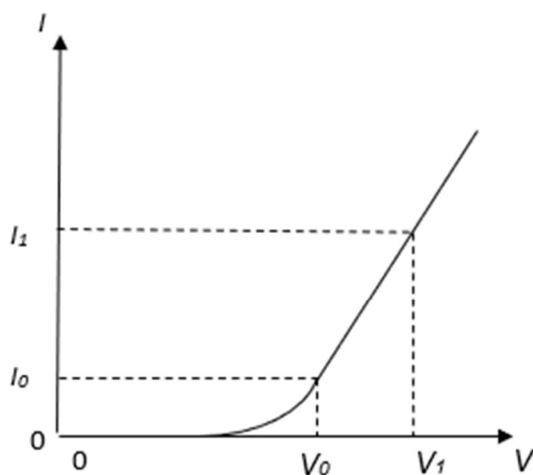The graph shows the current-voltage (I - V) characteristic of an electrical component.

What is the resistance of the component at potential difference V_1 and how does the resistance change, if at all, when the potential difference increases from V_0 to V_1 ?

	resistance at V_1	resistance change from V_0 to V_1
A	$\frac{V_1 - V_0}{I_1 - I_0}$	no change
B	$\frac{V_1 - V_0}{I_1 - I_0}$	decreases
C	$\frac{V_1}{I_1}$	no change
D	$\frac{V_1}{I_1}$	decreases