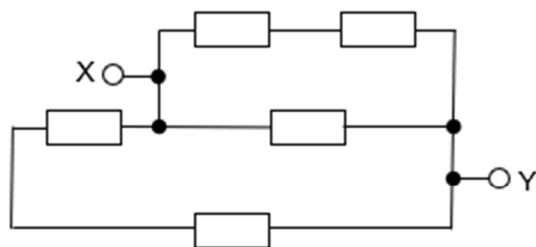


1

The circuit diagram shows a network of resistors each of resistance  $R$ .



What is the effective resistance between the points X and Y?

A  $\frac{2}{3}R$


B  $\frac{5}{8}R$

C  $\frac{R}{2}$

D  $\frac{2}{7}R$

2

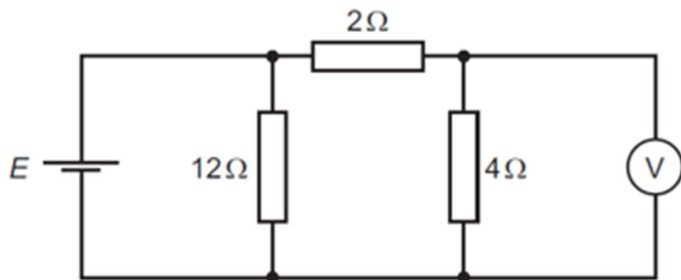A cell of electromotive force (e.m.f.)  $E$  and negligible internal resistance is connected into a circuit, as shown.



The voltmeter has a very high resistance and reads a potential difference  $V_{out}$ .

What is the ratio  $\frac{V_{out}}{E}$ ?

A  $\frac{1}{6}$


B  $\frac{1}{3}$

C  $\frac{1}{2}$

D  $\frac{2}{3}$

3

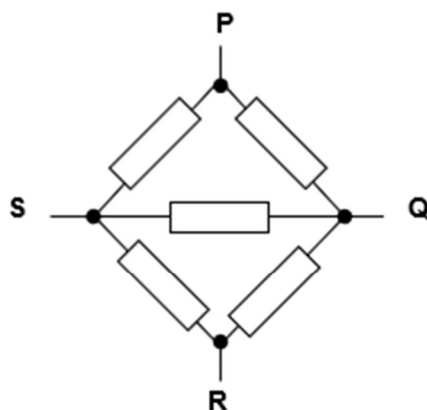Five resistors of equal resistance are connected as shown.




Which two points would give the maximum resistance?

**A** PQ**B** PR**C** PS**D** QS

4

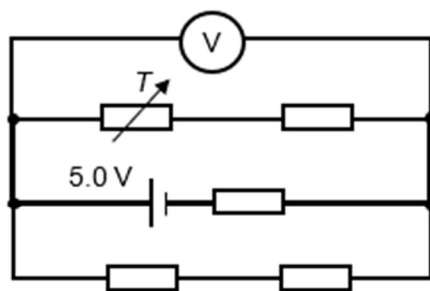A cell of e.m.f. 5.0 V and negligible internal resistance is connected to four similar resistors and a variable resistor  $T$ , as shown.




The resistance of each resistor is  $1.0 \text{ k}\Omega$  and the resistance of  $T$  is  $5.0 \text{ k}\Omega$ .

What is the reading of the ideal voltmeter?

**A** 0 V**B** 2.0 V**C** 3.0 V**D** 5.0 V

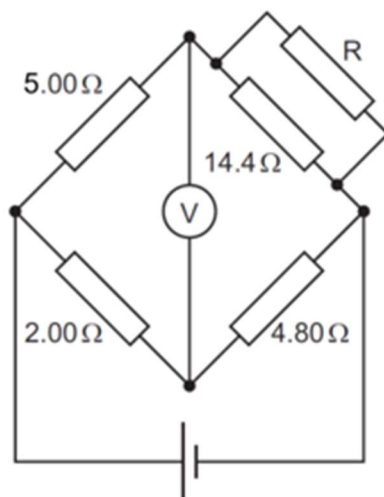
- 5 A cell of negligible internal resistance is connected to a network of resistors and a voltmeter, as shown.



The reading on the voltmeter is zero.

What is the resistance of resistor R?

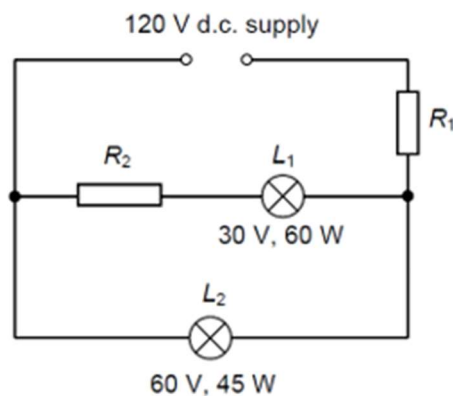- A**  $0\ \Omega$                       **B**  $2.40\ \Omega$                       **C**  $14.4\ \Omega$                       **D**  $72.0\ \Omega$
- 6 Two filament lamps  $L_1$  and  $L_2$  rated "30 V, 60 W" and "60 V, 45 W" respectively are connected across a 120 V d.c. supply of negligible internal resistance.




What is the value of the resistance  $R_1$  if both the lamps are operating at their rated powers?

- A**  $15\ \Omega$                       **B**  $22\ \Omega$                       **C**  $30\ \Omega$                       **D**  $80\ \Omega$

7

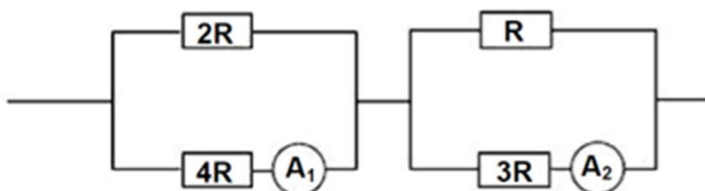The circuit shown in the diagram below is connected to a power supply.




If ammeter  $A_1$  reads 6.0 A, what is the reading on ammeter  $A_2$ ?

- A** 13.5 A      **B** 6.0 A      **C** 4.5 A      **D** 2.3 A

8

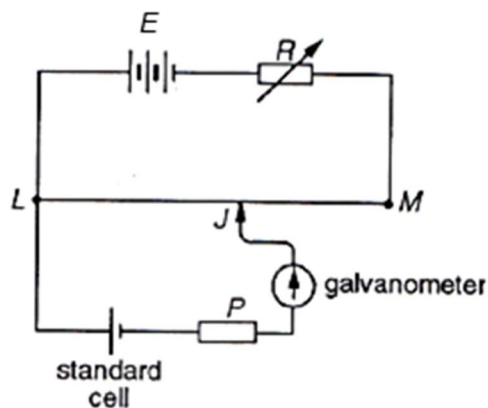
No balance point can be found for the potentiometer shown below.



Which of the following may allow a balance point to be found?


- A** increasing the resistance of the rheostat  $R$ .  
**B** replacing the resistance wire  $LM$  with one of higher resistance.  
**C** reversing the polarity of the driver cell  $E$ .  
**D** replacing the resistor  $P$  with one of higher resistance.

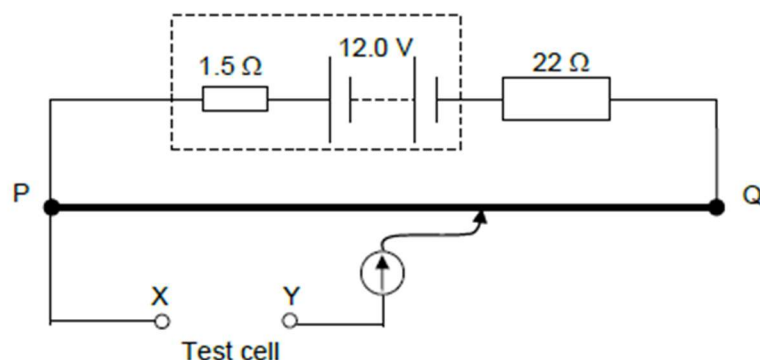- 9 A student attempts to measure the e.m.f. of a test cell using a potentiometer circuit as shown in the diagram.



The wire PQ has a resistance of  $3.0\ \Omega$  and the driver cell has an e.m.f. of  $12.0\ \text{V}$ . He was unable to obtain an observable balance length on PQ when he connected the circuit. The tutor he consulted told him that the test cell has an e.m.f. of a few millivolts. What could he do in order to obtain an observable balance length?


- A** Reversed the polarity of the test cell at XY.  
**B** Use a driver cell of e.m.f.  $20\ \text{V}$ .  
**C** Change the resistance of the connected resistor to  $1\ \text{k}\Omega$ .  
**D** Change the wire PQ to a wire of resistance  $20\ \Omega$ .
- 10 Four resistors  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  are connected in a circuit.  $R_2$  is in series with an ammeter, while  $R_3$  is in series with switch S. Switch S is initially open.

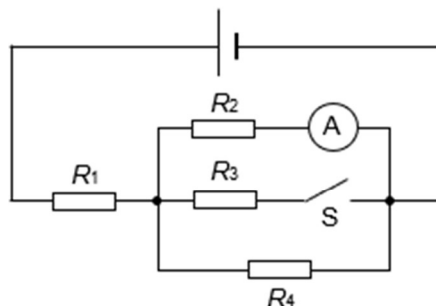

Which of the following changes, when made independently, would increase the reading on the ammeter?

- A** Increase  $R_1$       **B** Increase  $R_2$       **C** Increase  $R_4$       **D** Close S

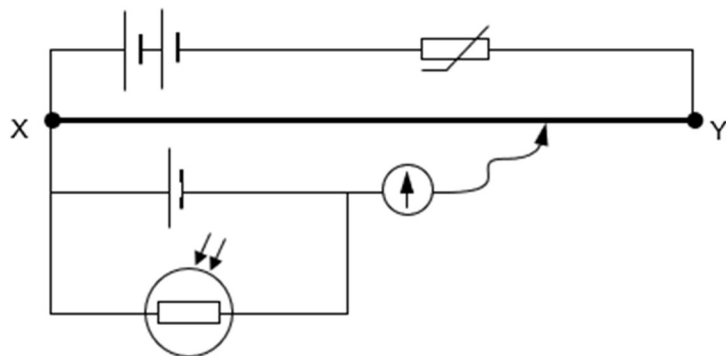- 11 A NTC thermistor and a light-dependent resistor are connected in a potentiometer circuit. The batteries have finite internal resistance. XY is a resistance wire.




Which row of environmental conditions maximizes the balance length of the potentiometer?





	temperature	lighting condition
A	high	bright
B	high	dark
C	low	bright
D	low	dark

12

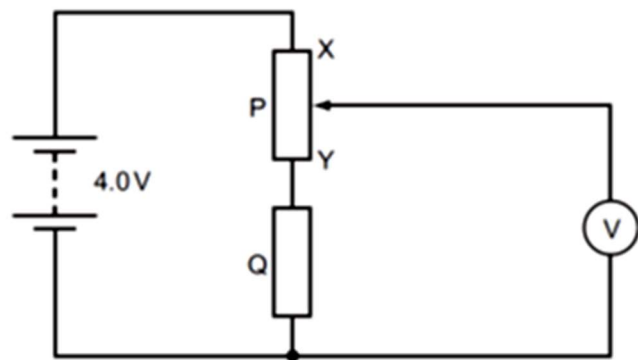In the circuit below, P is a potentiometer of total resistance  $10\ \Omega$  and Q is a fixed resistor of resistance  $10\ \Omega$ . The battery has an e.m.f. of  $4.0\text{ V}$  and negligible internal resistance. The voltmeter has a very high resistance. The slider on the potentiometer is moved from X to Y and a graph of voltmeter reading  $V$  is plotted against slider position.




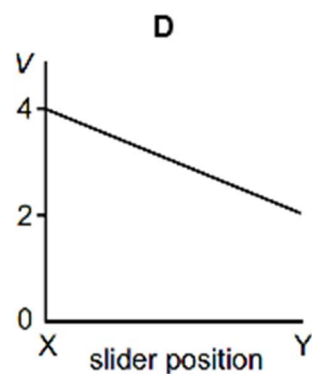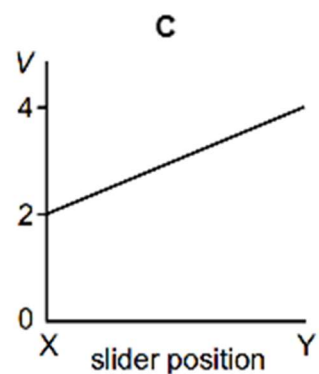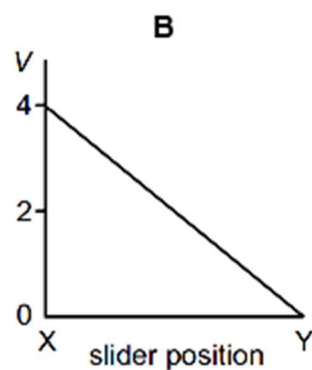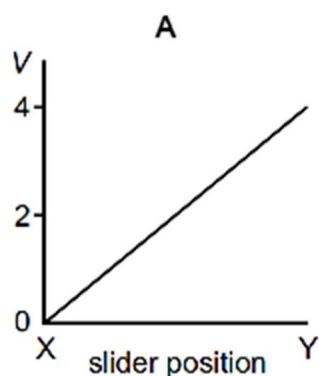Which of the following shows the correct graph obtained?



13

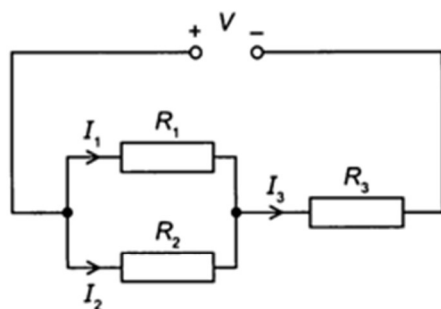A power supply giving an output potential difference  $V$  is connected as shown to resistors  $R_1$ ,  $R_2$  and  $R_3$ . The currents in the circuit are  $I_1$ ,  $I_2$ , and  $I_3$ .



A student wishes to calculate the value of  $R_2$ .


Which group of values would be enough to enable the student to find  $R_2$ ?

- A  $I_1$ ,  $I_2$ ,  $I_3$  and  $R_3$
- B  $I_1$ ,  $I_2$ ,  $I_3$  and  $V$
- C  $I_2$ ,  $R_1$ ,  $R_3$ , and  $V$
- D  $I_3$ ,  $R_1$ ,  $R_3$ , and  $V$

14

A potentiometer circuit is used to determine the unknown electromotive force (e.m.f.) of a cell X.

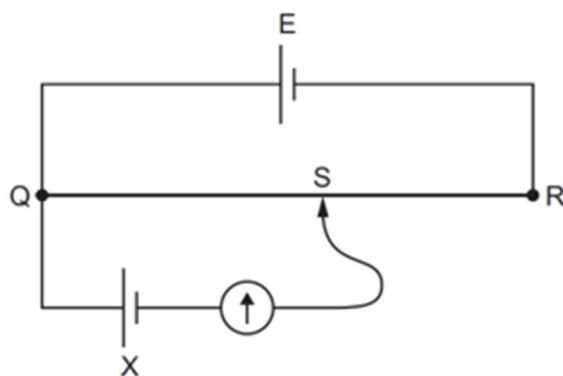In the circuit shown, E is a cell with an e.m.f. that is known accurately. QR is the potentiometer wire, which has a movable contact S. Contact S is connected to a galvanometer and to cell X.




What is not a necessary requirement to determine the e.m.f. of X from the circuit?

- A The e.m.f. of cell X must be lower than the e.m.f. of cell E.
- B The internal resistance of cell X must be known.
- C The lengths QS and QR must be determined accurately.
- D The resistance of the wire QR must be proportional to its length.



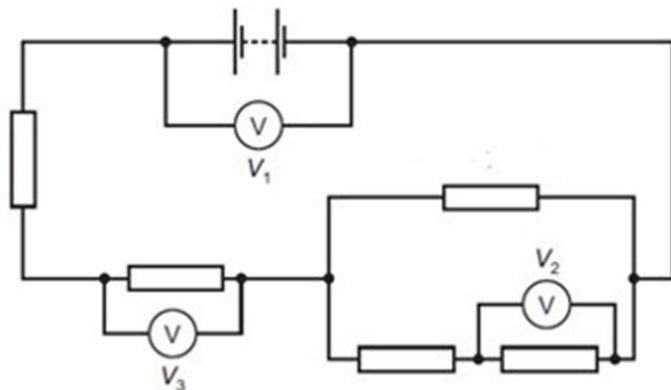- 15 In the circuit shown, all the resistors are identical.



The reading  $V_1$  is 8.0 V and the reading  $V_2$  is 1.0 V.

What is the reading  $V_3$ ?

- A** 1.5 V      **B** 3.0 V      **C** 4.5 V      **D** 6.0 V

- 16

Two wires each of length  $L$  are used to connect an a.c. power supply to a lamp. The a.c. power supply has a peak voltage of 12 V and negligible internal resistance.





The r.m.s potential difference across the lamp is 7.00 V. The r.m.s current in the wires is 2.50 A. Each wire is made of a metal of resistivity  $1.70 \times 10^{-8} \Omega \text{ m}$  and has a cross-sectional area of  $6.00 \times 10^{-7} \text{ m}^2$ .

What is the length  $L$  of each wire?

- A** 10.5 m      **B** 21.0 m      **C** 35.3 m      **D** 58.8 m


17

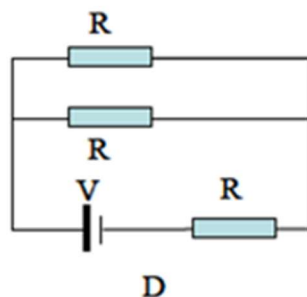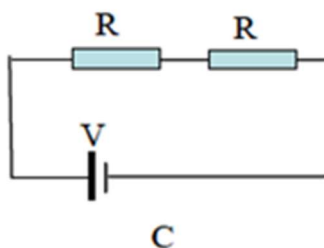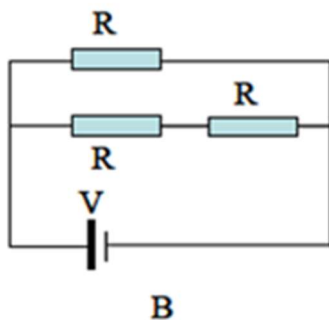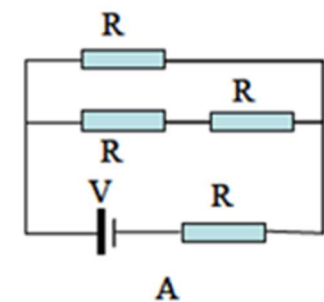Four circuits are shown below. The batteries all have the same voltage  $V$  and all resistors have the same resistance  $R$ . In which circuit does the battery produce the most power?



18

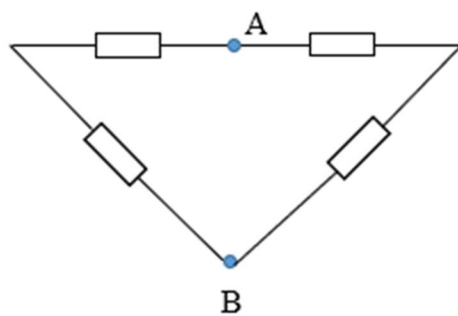Four identical resistors, each of resistance  $R$ , are connected as shown in the diagram below.



What is the effective resistance between points A and B?

A  $\frac{1}{2}R$


B  $R$

C  $\frac{3}{2}R$


D  $2R$

19

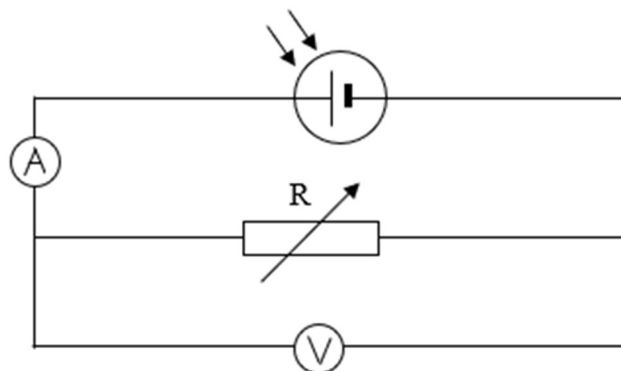A photovoltaic cell is connected to a variable resistor  $R$  as shown below.



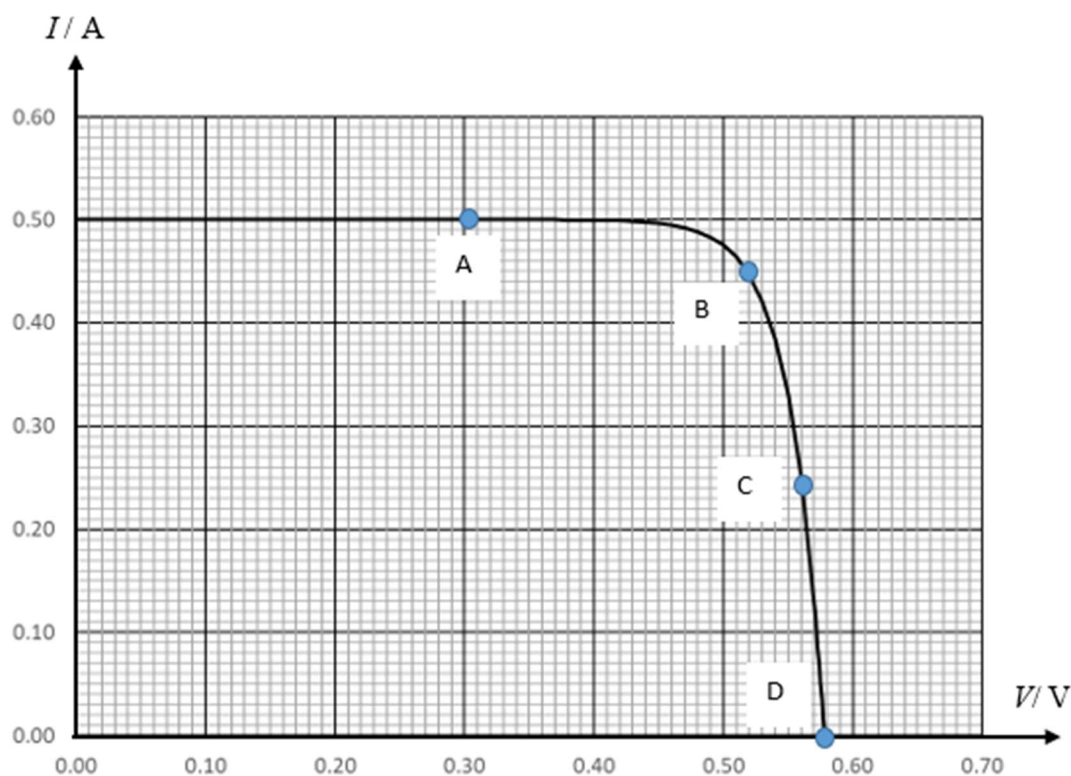As the resistance of the variable resistor is adjusted, the current  $I$  and voltage  $V$  recorded by the ammeter and voltmeters are recorded. The variation with the voltage  $V$  of current  $I$  is shown in the graph below.



Approximately at which point is the power delivered to the resistor a maximum?